
Elec 4700 Assignment 4

Table of Contents

| | |
|--|----|
| Joel Demetre (100943543) | 1 |
| Part 2 A) | 1 |
| Part C) Plot of AC Analysis | 3 |
| Part D and Part E | 6 |
| Question 2 | 12 |
| Part A) Updated C Matrix | 12 |
| Part B) Vout with Noise | 13 |
| Part C and D) Fourier Transform with Noise | 14 |
| Part E) 3 Plots with Different Cout's | 15 |
| Part F) 2 Plots with different time steps | 20 |
| Question 4 | 24 |
| Part A) Change to Simulator | 24 |

Joel Demetre (100943543)

```
clear all;
close all;
%Parameters
G1 = 1;
Cx = 0.25;
G2 = 1/2;
L = 0.2;
G3 = 1/10;
Alpha = 100;
G4 = 1/0.1;
G0 = 1/1000;
```

Part 2 A)

The C and G Matrices

```
C = [ 0 0 0 0 0 0 0 0;
      -Cx Cx 0 0 0 0 0 0;
      0 0 -L 0 0 0 0 0;
      0 0 0 0 0 0 0 0;
      0 0 0 0 0 0 0 0;
      0 0 0 0 0 0 0 0;
      0 0 0 0 0 0 0 0;];


G = [ 1 0 0 0 0 0 0 0;
      -G2 G1+G2 -1 0 0 0 0 0;
      0 1 0 -1 0 0 0 0;
```

```
    0 0 -1 G3 0 0 0;
    0 0 0 0 -Alpha 1 0;
    0 0 0 G3 -1 0 0;
    0 0 0 0 0 -G4 G4+G0;];

F = [0; 0; 0; 0; 0; 0; 0; 0];

% Part B) Plot of DC Sweep
counter = 1;
for i = -10:0.2:10
    F(1) = i;
    V = G\F;
    out(counter , 1) = i;
    out(counter , 2) = V(7);
    out(counter , 3) = V(4);
    counter = counter + 1;
end
figure;
title('DC Analysis V3 and V0');
xlabel('DC Voltage (V)');
ylabel('Response Voltage (V)');
hold on;
grid on;
grid minor;
plot(out(:,1), out(:,2), 'r');
plot(out(:,1), out(:,3), 'b');
legend('V0', 'V3');

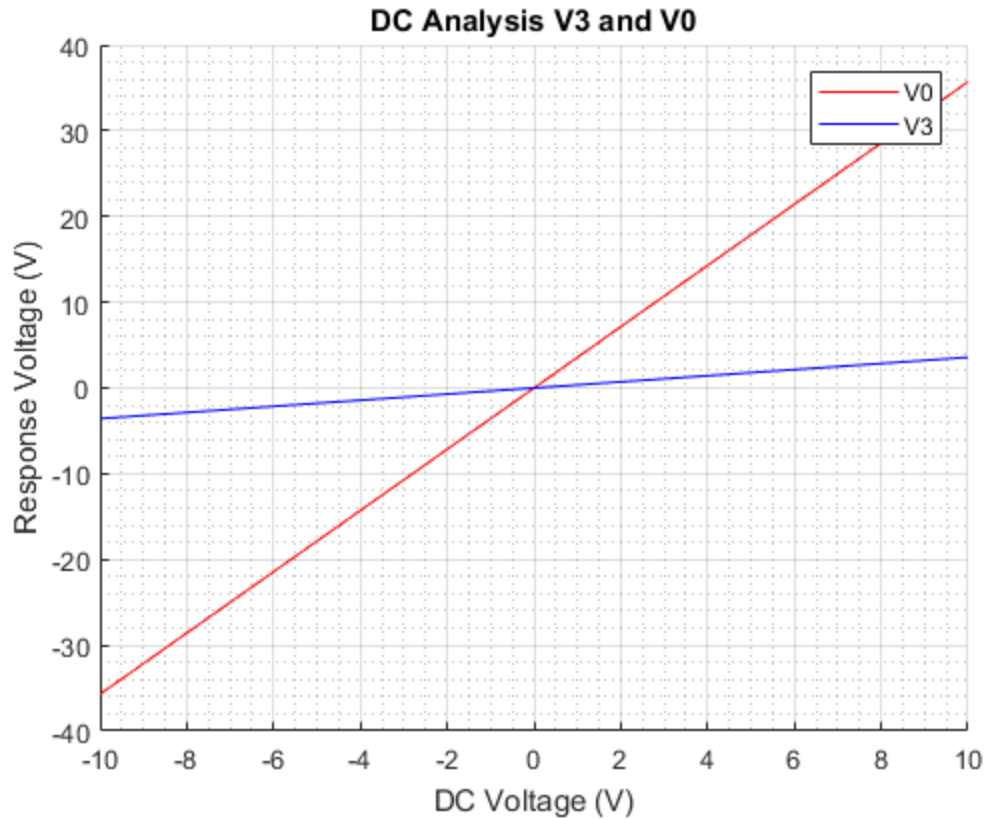%Part C
clear out
counter = 1;
for i = 0:1:10000
    F(1) = 10;
    V = (G + i*C)\F;
    out(counter , 1) = i;
    out(counter , 2) = V(7);
    out(counter , 3) = V(7)/V(1);
    counter = counter + 1;
end
```



Part C) Plot of AC Analysis

```
figure;
title('Frequency Analysis V0');
xlabel('Frequency (Hz)');
ylabel('Response Voltage (V)');
hold on;
grid on;
grid minor;
plot(out(:,1), out(:,2), 'r');
legend('V0');
hold off;


figure;



semilogx(out(:,1), out(:,3));
legend('Gain');
title('Frequency Analysis of Gain');
xlabel('Frequency (Hz)');
ylabel('Gain (dB)');
hold on;
grid on;
grid minor;
```

```

clear out
counter = 1;
for i = 1:100
    C(2,1) = -normrnd(Cx, 0.05);
    C(2,2) = normrnd(Cx, 0.05);
    F(1) = 10;
    V = (G + pi*C)\F;
    out(counter , 1) = i;
    out(counter , 2) = 20*log10(V(7)/V(1));
    counter = counter + 1;
end
figure;
title('Histogram of Gain');
xlabel('Voltage Gain');
ylabel('Frequency');
hold on;
grid on;
grid minor;
histogram(out(:,2));
legend('Voltage Gain');

```

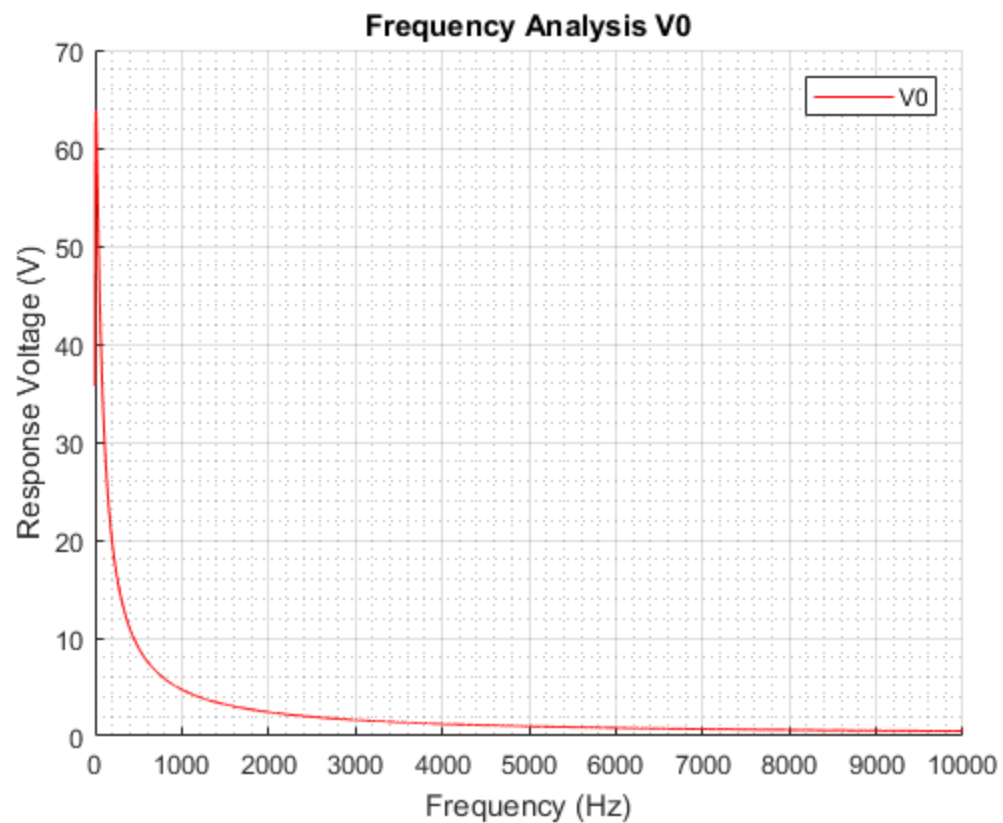

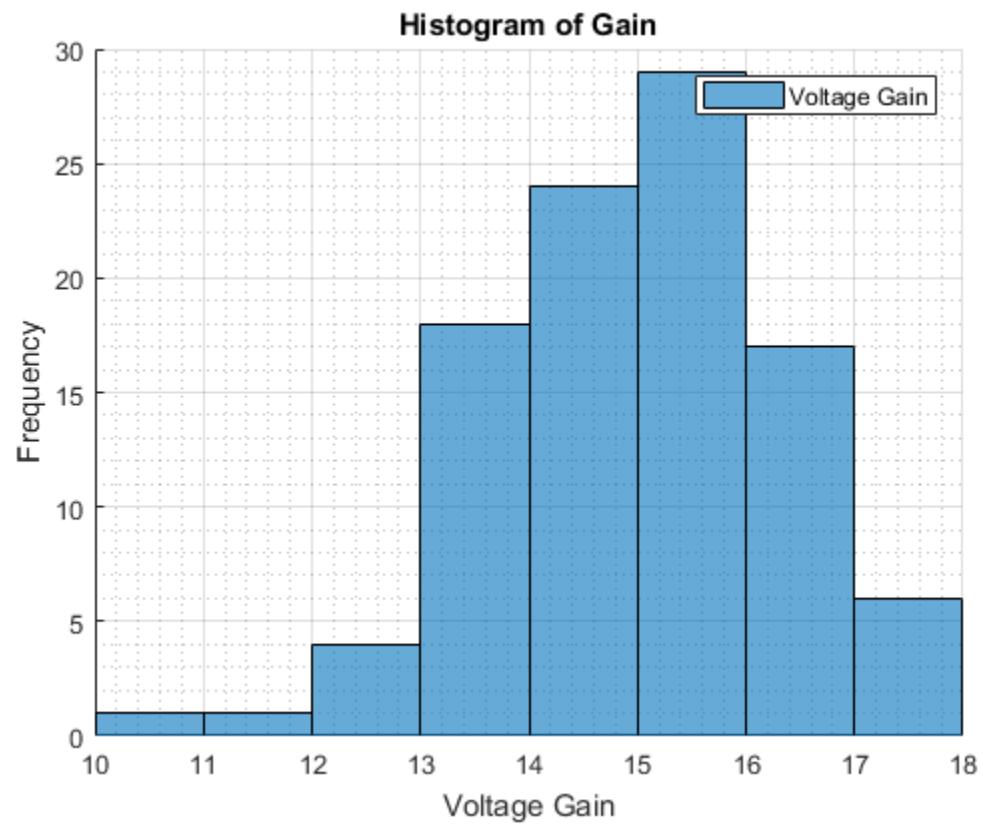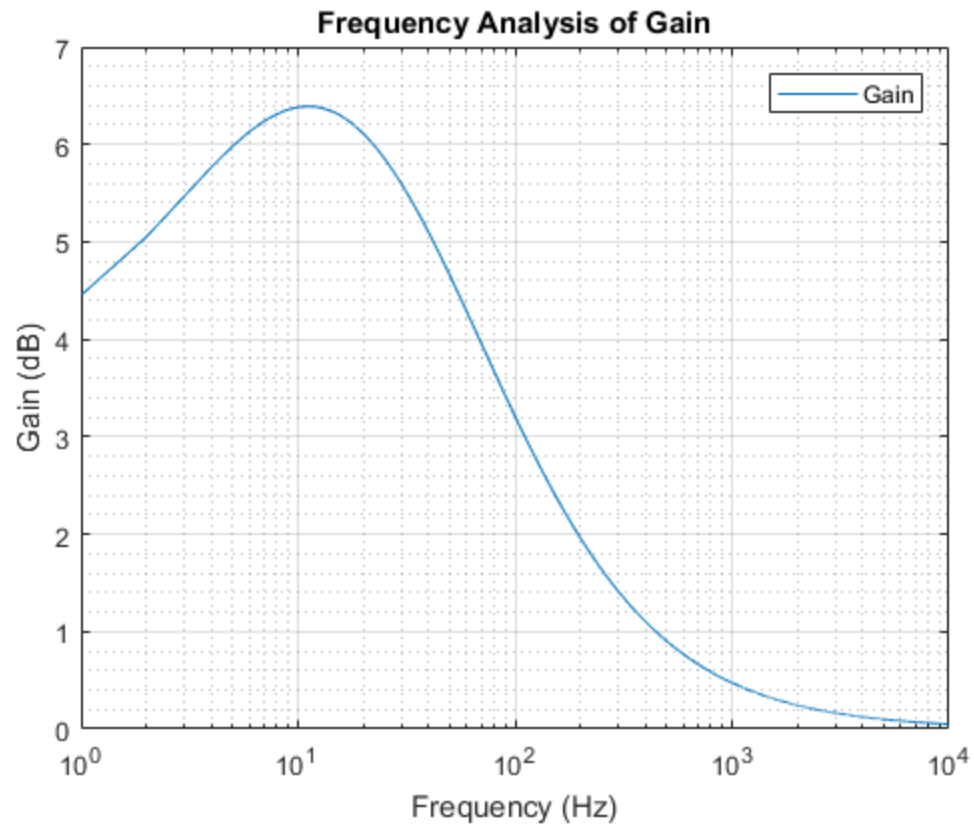

Part D and Part E

The Analysis of the V_{in} and V_{out} as well as the fourier transform for various functions such as step transition, gaussian pulse and sine function.

```
L = 1000;

clear out;
deltaT = 0.001;
A = (C/deltaT + G);
F = [0; 0; 0; 0; 0; 0; 0; 0];
Vold = [1; 0; 0; 0; 0; 0; 0; 0];
counter = 1;
for i = 0.001:deltaT:L*0.001
    if round(i*1000)>30
        F(1) = 1;
    end
    vNew = inv(A)*(C*Vold./deltaT + F);
    Vold = vNew;
    out(counter , 1) = i;
    out(counter , 2) = vNew(7);
    out(counter , 3) = vNew(1);
    counter = counter + 1;
end
figure;
hold on;
grid on;
grid minor;
title('Step Function');
xlabel('Time (s)');
ylabel('Voltage (V)');
plot(out(:,1), out(:,2));
plot(out(:,1), out(:,3));
legend('Output', 'Input');
hold off;

figure;

Fs = 1000;

n = 2^nextpow2(L);
Y = fft(out(:,2),n);
Y = fftshift(Y);
fshift = (-n/2:n/2-1)*(Fs/n);
powershift = abs(Y).^2/n;
f = Fs*(0:(n/2))/n;
P = abs(Y/n);
semilogy(fshift, powershift) ;
hold on;
grid on;
grid minor;
title('Step Function');
xlabel('Frequency (Hz)');
```

```
ylabel('Voltage (V)');

Y = fft(out(:,3),n);
Y = fftshift(Y);
fshift = (-n/2:n/2-1)*(Fs/n);
powershift = abs(Y).^2/n;
f = Fs*(0:(n/2))/n;
P = abs(Y/n);
semilogy(fshift, powershift) ;
legend('Output', 'Input');
hold off;

clear out;
deltaT = 0.001;
A = (C/deltaT + G);
F = [0; 0; 0; 0; 0; 0; 0; 0];
Vold = [1; 0; 0; 0; 0; 0; 0; 0];
counter = 1;
for i = 0.001:deltaT:L*0.001
    F(1) = sin(2*pi*i/(0.03));
    vNew = inv(A)*(C*Vold./deltaT + F);
    Vold = vNew;
    out(counter , 1) = i;
    out(counter , 2) = vNew(7);
    out(counter , 3) = vNew(1);
    counter = counter + 1;
end
figure;
hold on;
grid on;
grid minor;
title('Sine Wave');
xlabel('Time (s)');
ylabel('Voltage (V)');
plot(out(:,1), out(:,2));
plot(out(:,1), out(:,3));
legend('Output', 'Input');
hold off;

figure;

Fs = 1000;

n = 2^nextpow2(L);
Y = fft(out(:,2),n);
Y = fftshift(Y);
fshift = (-n/2:n/2-1)*(Fs/n);
powershift = abs(Y).^2/n;
f = Fs*(0:(n/2))/n;
P = abs(Y/n);
semilogy(fshift, powershift) ;
hold on;
```

```
grid on;
grid minor;
title('Sine Wave');
xlabel('Frequency (Hz)');
ylabel('Voltage (V)');
Y = fft(out(:,3),n);
Y = fftshift(Y);
fshift = (-n/2:n/2-1)*(Fs/n);
powershift = abs(Y).^2/n;
f = Fs*(0:(n/2))/n;
P = abs(Y/n);
semilogy(fshift, powershift) ;
legend('Output', 'Input');
hold off;

clear out;
deltaT = 0.001;
A = (C/deltaT + G);
F = [0; 0; 0; 0; 0; 0; 0; 0];
Vold = [1; 0; 0; 0; 0; 0; 0; 0];
counter = 1;
for i = 0.001:deltaT:L*0.001
    F(1) = normpdf(i,0.06,0.03)/13.2981;
    vNew = inv(A)*(C*Vold./deltaT + F);
    Vold = vNew;
    out(counter , 1) = i;
    out(counter , 2) = vNew(7);
    out(counter , 3) = vNew(1);
    counter = counter + 1;
end
figure;
hold on;
grid on;
grid minor;
title('Gaussian Pulse');
xlabel('Time (s)');
ylabel('Voltage (V)');
plot(out(:,1), out(:,2));
plot(out(:,1), out(:,3));
legend('Output', 'Input');
hold off;

figure;

Fs = 1000;


n = 2^nextpow2(L);
Y = fft(out(:,2),n);
Y = fftshift(Y);
fshift = (-n/2:n/2-1)*(Fs/n);
powershift = abs(Y).^2/n;
f = Fs*(0:(n/2))/n;
```







```


P = abs(Y/n);
semilogy(fshift, powershift) ;
hold on;
grid on;
grid minor;
title('Gaussian Pulse');
xlabel('Frequency (Hz)');
ylabel('Voltage (V)');
Y = fft(out(:,3),n);
Y = fftshift(Y);
fshift = (-n/2:n/2-1)*(Fs/n);
powershift = abs(Y).^2/n;
f = Fs*(0:(n/2))/n;
P = abs(Y/n);
semilogy(fshift, powershift) ;
legend('Output', 'Input');
hold off;

```

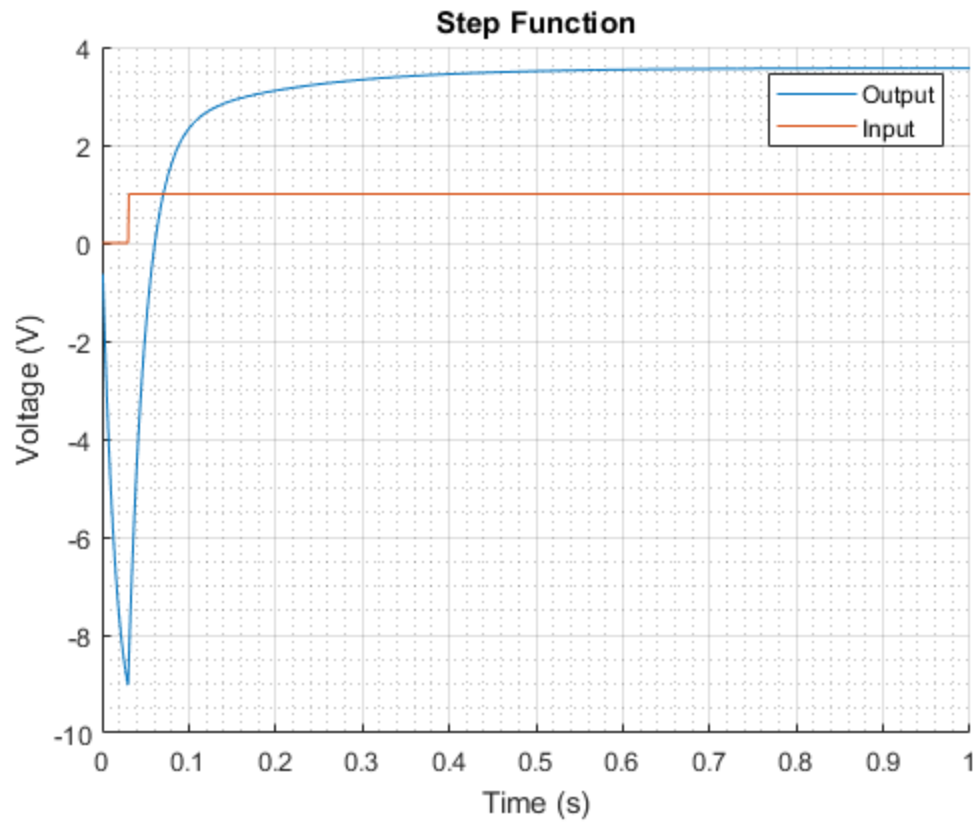

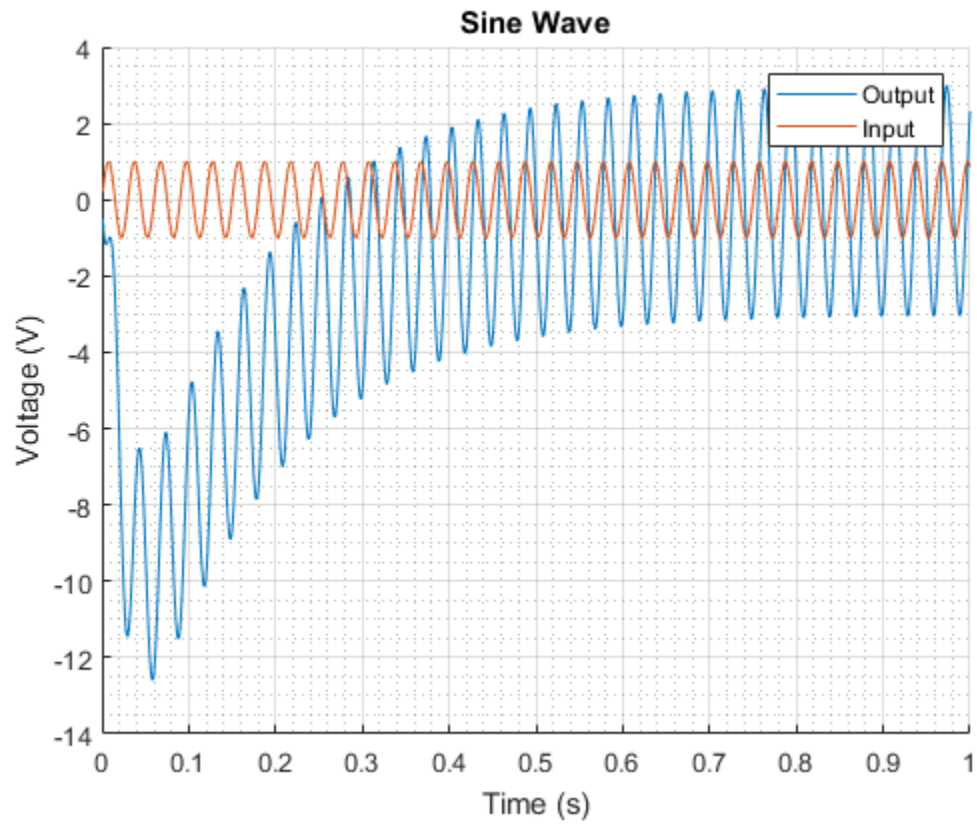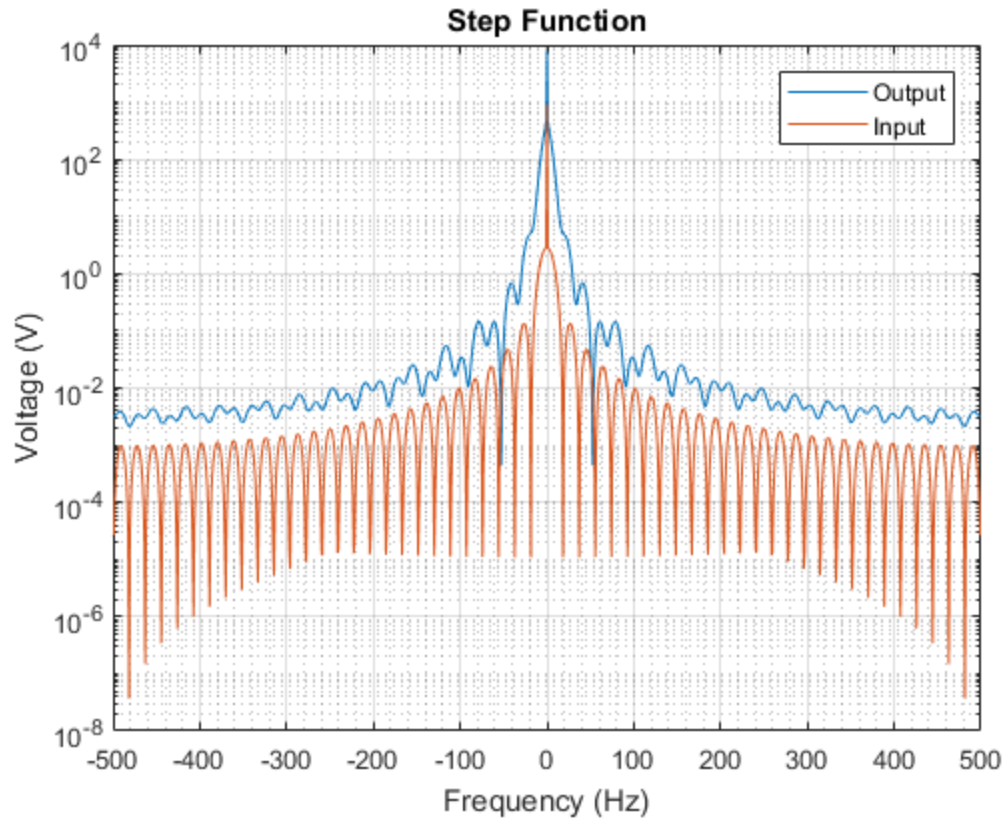

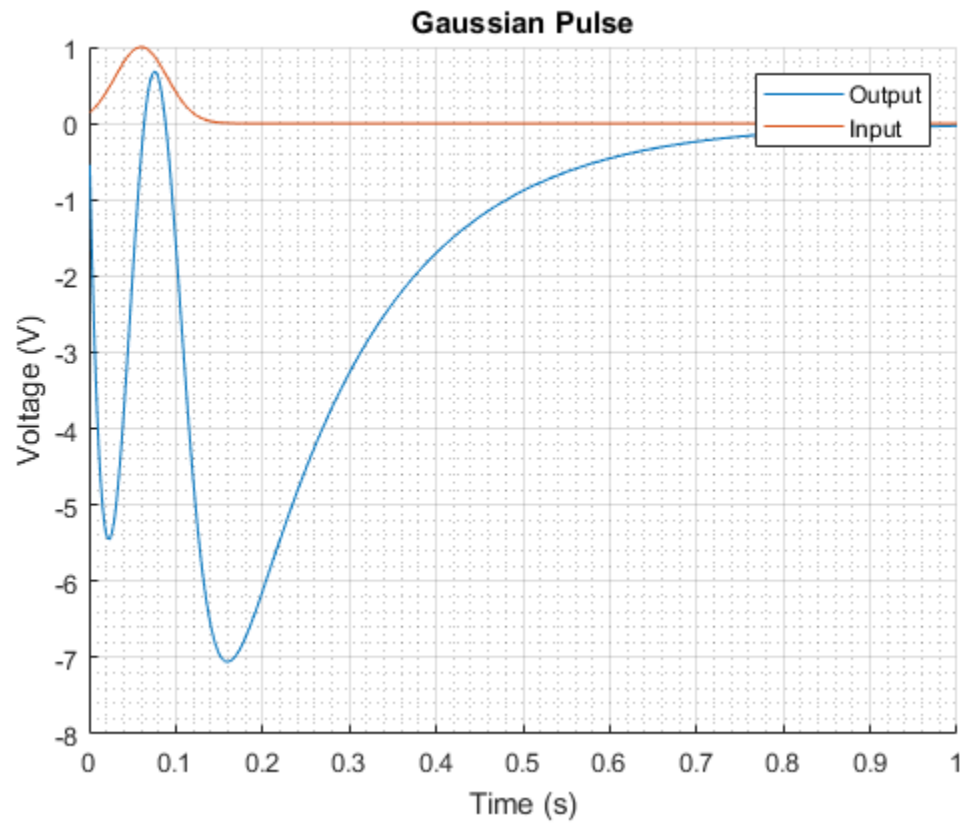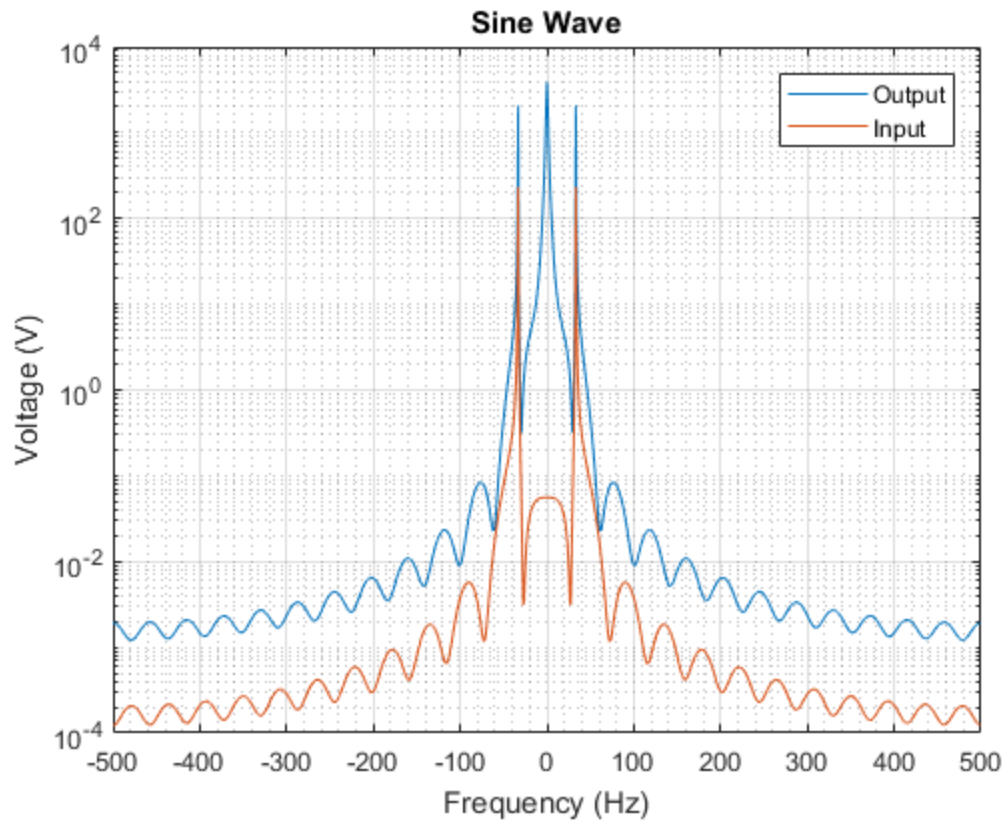

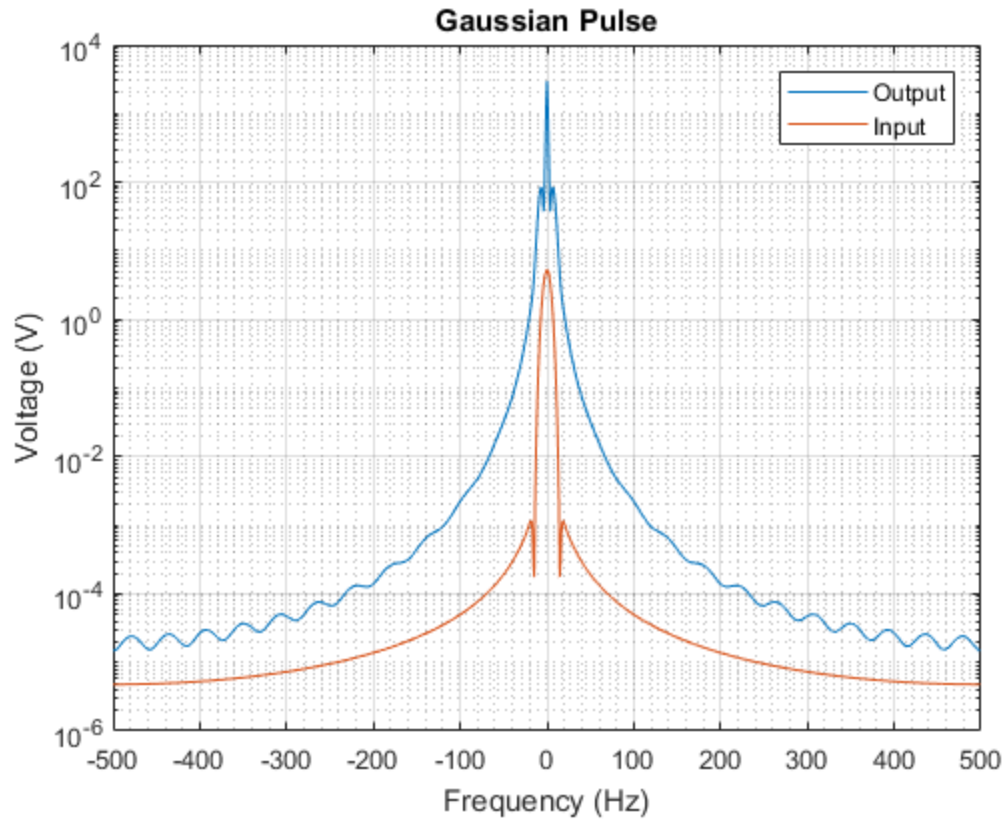

Question 2

```
clear all;
close all;

%Parameters
G1 = 1;
Cx = 0.25;
G2 = 1/2;
L = 0.2;
G3 = 1/10;
Alpha = 100;
G4 = 1/0.1;
G0 = 1/1000;
Cn = 0.00001;
```

Part A) Updated C Matrix

```
C = [ 0 0 0 0 0 0 0 0 0;
      -Cx Cx 0 0 0 0 0 0 0;
      0 0 -L 0 0 0 0 0 0;
      0 0 0 0 0 0 0 0 0;
      0 0 0 0 0 0 0 0 0;
      0 0 0 0 0 0 0 0 0;
```

```
0 0 0 -Cn 0 0 0 0;
0 0 0 0 0 0 0 0;];


G = [ 1 0 0 0 0 0 0 0;
      -G2 G1+G2 -1 0 0 0 0 0;
      0 1 0 -1 0 0 0 0;
      0 0 -1 G3 0 0 0 0;
      0 0 0 0 -Alpha 1 0 0;
      0 0 0 G3 -1 0 0 1;
      0 0 0 0 0 -G4 G4+G0 0;
      0 0 0 0 0 0 0 1;];

F = [0; 0; 0; 0; 0; 0; 0; 0];

deltaT = 0.001;
A = (C/deltaT + G);
Vold = [1; 0; 0; 0; 0; 0; 0; 0];
counter = 1;
L = 1000;
for i = 0.001:deltaT:L*0.001
    F(1) = normpdf(i,0.06,0.03)/13.2981;
    F(8) = normrnd(0.001, 0.0002);
    vNew = inv(A)*(C*Vold./deltaT + F);
    Vold = vNew;
    out(counter , 1) = i;
    out(counter , 2) = vNew(7);
    out(counter , 3) = vNew(1);
    counter = counter + 1;
end
```

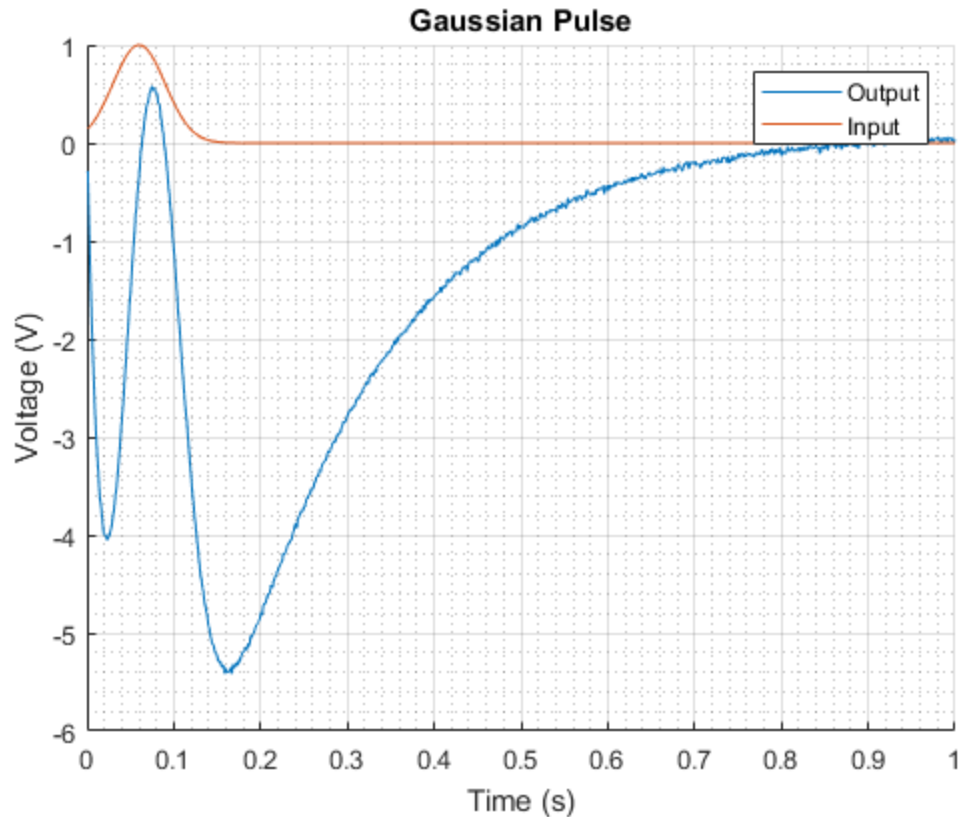Part B) Vout with Noise

```
figure;
hold on;
grid on;
grid minor;
title('Gaussian Pulse');
xlabel('Time (s)');
ylabel('Voltage (V)');
plot(out(:,1), out(:,2));
plot(out(:,1), out(:,3));
legend('Output', 'Input');
hold off;
```



Part C and D) Fourier Transform with Noise

```
figure;


Fs = 1000;

n = 2^nextpow2(L);
Y = fft(out(:,2),n);
Y = fftshift(Y);
fshift = (-n/2:n/2-1)*(Fs/n);
powershift = abs(Y).^2/n;
f = Fs*(0:(n/2))/n;
P = abs(Y/n);
semilogy(fshift, powershift) ;
hold on;
grid on;
grid minor;
title('Gaussian Pulse');
xlabel('Frequency (Hz)');
ylabel('Voltage (V)');
Y = fft(out(:,3),n);
Y = fftshift(Y);
fshift = (-n/2:n/2-1)*(Fs/n);
powershift = abs(Y).^2/n;
f = Fs*(0:(n/2))/n;
```

```

P = abs(Y/n);
semilogy(fshift, powershift) ;
legend('Output', 'Input');
hold off;

```

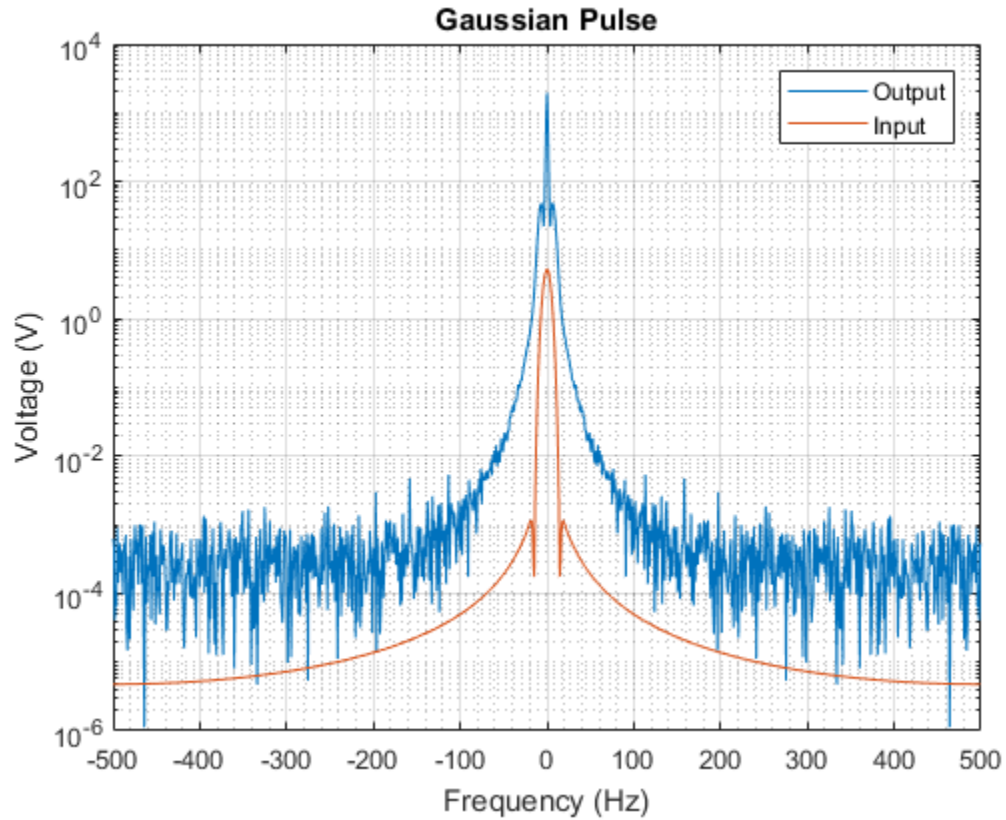

Part E) 3 Plots with Different Cout

With a higher C_n the bandwidth becomes more broad

```

for zz = 1:3
    Cn = 0.00001*zz^7;

    C = [ 0 0 0 0 0 0 0 0 0;
          -Cx Cx 0 0 0 0 0 0 0;
          0 0 -L 0 0 0 0 0 0;
          0 0 0 0 0 0 0 0 0;
          0 0 0 0 0 0 0 0 0;
          0 0 0 0 0 0 0 0 0;
          0 0 0 -Cn 0 0 0 0 0;
          0 0 0 0 0 0 0 0 0;];

    G = [ 1 0 0 0 0 0 0 0 0;
          -G2 G1+G2 -1 0 0 0 0 0 0;
          0 1 0 -1 0 0 0 0 0;

```

```
0 0 -1 G3 0 0 0 0;
0 0 0 0 -Alpha 1 0 0;
0 0 0 G3 -1 0 0 1;
0 0 0 0 0 -G4 G4+G0 0;
0 0 0 0 0 0 0 1;];

deltaT = 0.001;
A = (C/deltaT + G);
F = [0; 0; 0; 0; 0; 0; 0; 0; 0];
Vold = [1; 0; 0; 0; 0; 0; 0; 0; 0];
counter = 1;
for i = 0.001:deltaT:L*0.001
    F(1) = normpdf(i,0.06,0.03)/13.2981;
    F(8) = normrnd(0.001, 0.0002);
    vNew = inv(A)*(C*Vold./deltaT + F);
    Vold = vNew;
    out(counter , 1) = i;
    out(counter , 2) = vNew(7);
    out(counter , 3) = vNew(1);
    counter = counter + 1;
end
figure;
hold on;
grid on;
grid minor;
title(strcat('Bandwidth Changing-Cn:', num2str(Cn)));
xlabel('Time (s)');
ylabel('Voltage (V)');
plot(out(:,1), out(:,2));
plot(out(:,1), out(:,3));
legend('Output', 'Input');
hold off;


figure;



Fs = 1000;



n = 2^nextpow2(L);
Y = fft(out(:,2),n);
Y = fftshift(Y);
fshift = (-n/2:n/2-1)*(Fs/n);
powershift = abs(Y).^2/n;
f = Fs*(0:(n/2))/n;
P = abs(Y/n);
semilogy(fshift, powershift) ;
hold on;
grid on;
grid minor;
title(strcat('Bandwidth Changing-Cn:', num2str(Cn)));
xlabel('Frequency (Hz)');
ylabel('Voltage (V)');
Y = fft(out(:,3),n);
```


```
Y = fftshift(Y);  
fshift = (-n/2:n/2-1)*(Fs/n);  
powershift = abs(Y).^2/n;  
f = Fs*(0:(n/2))/n;  
P = abs(Y/n);  
semilogy(fshift, powershift) ;  
legend('Output', 'Input');  
hold off;
```

```
end
```

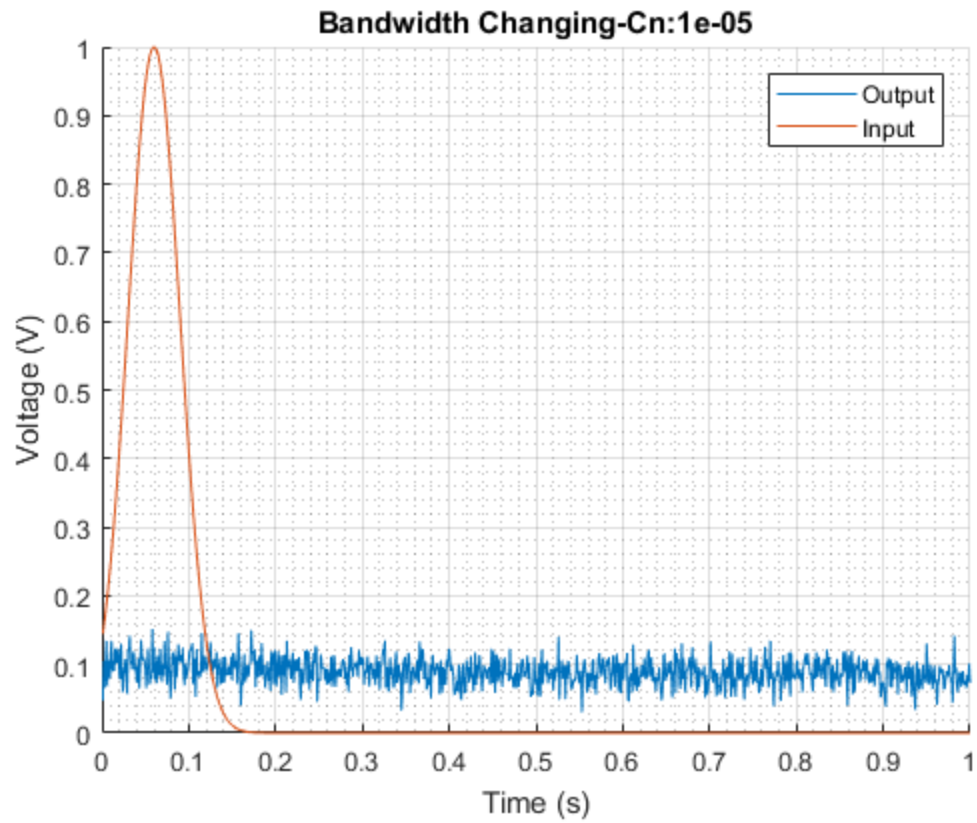

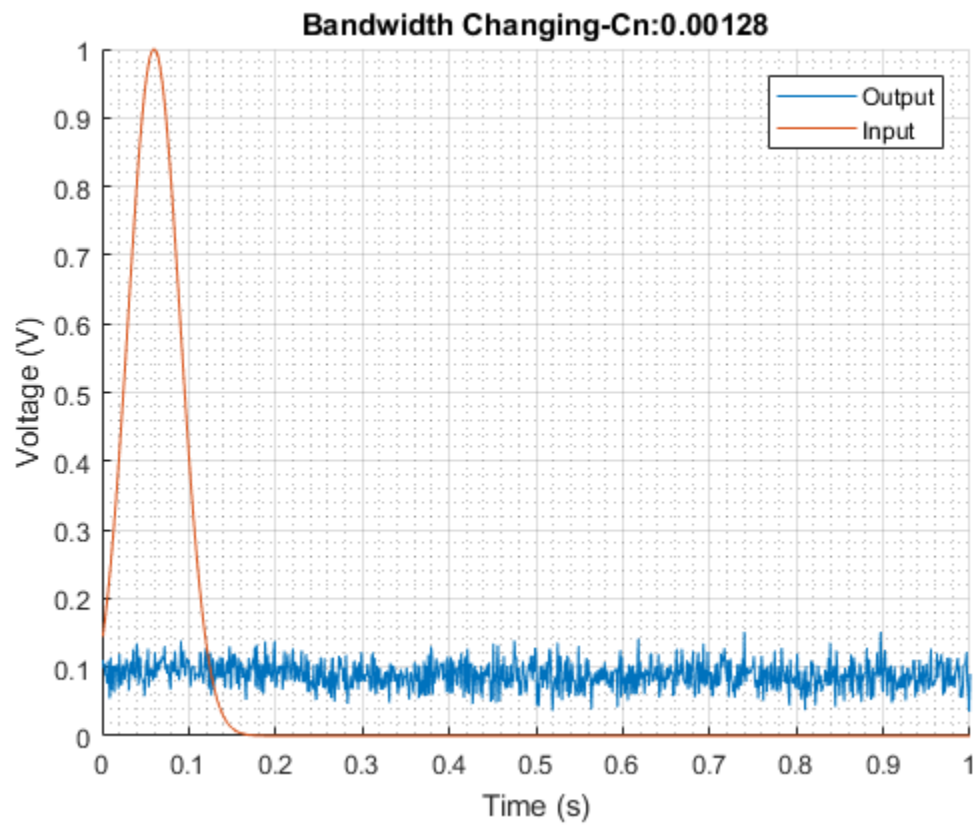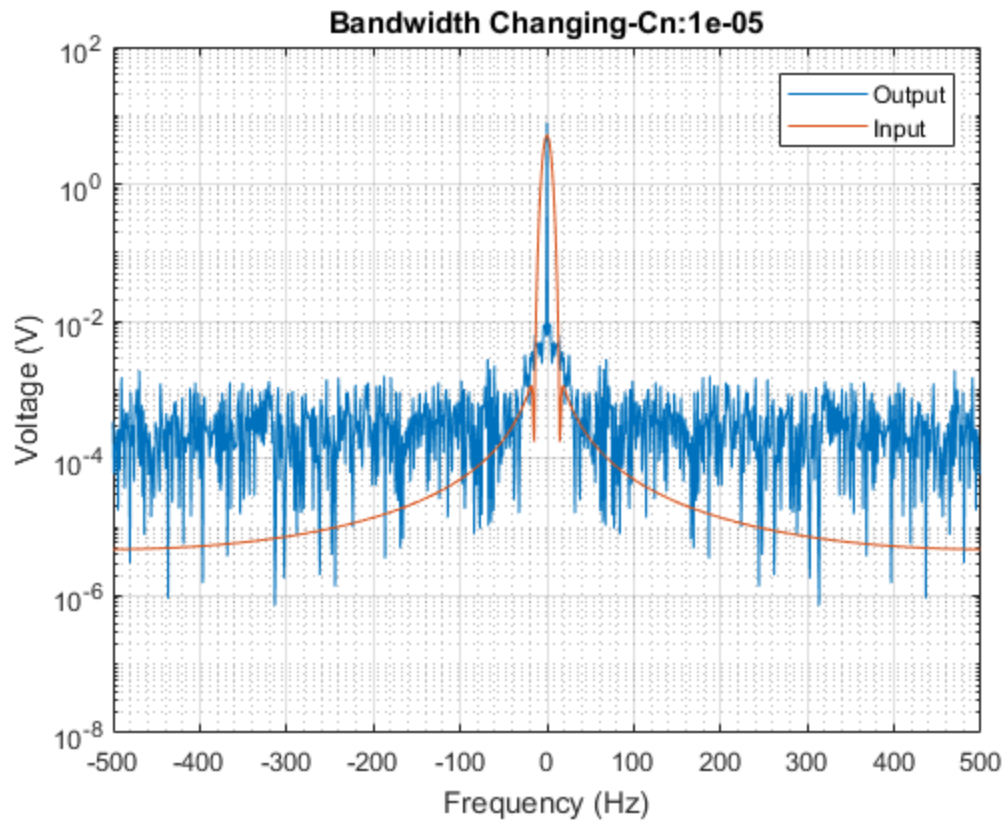

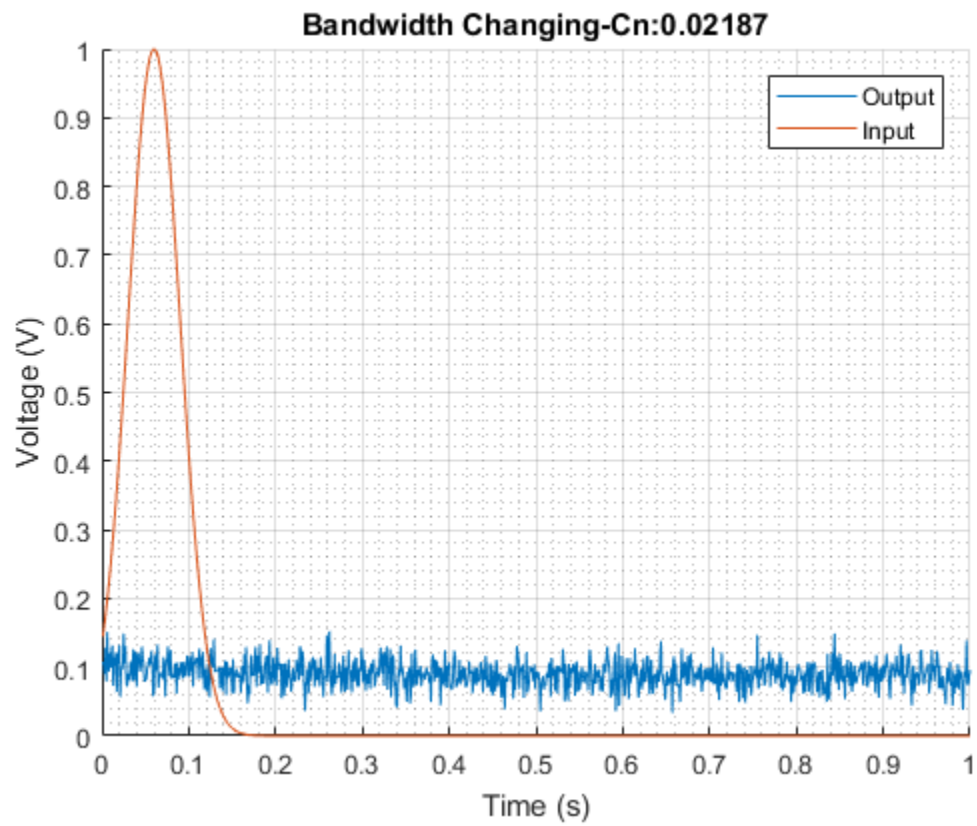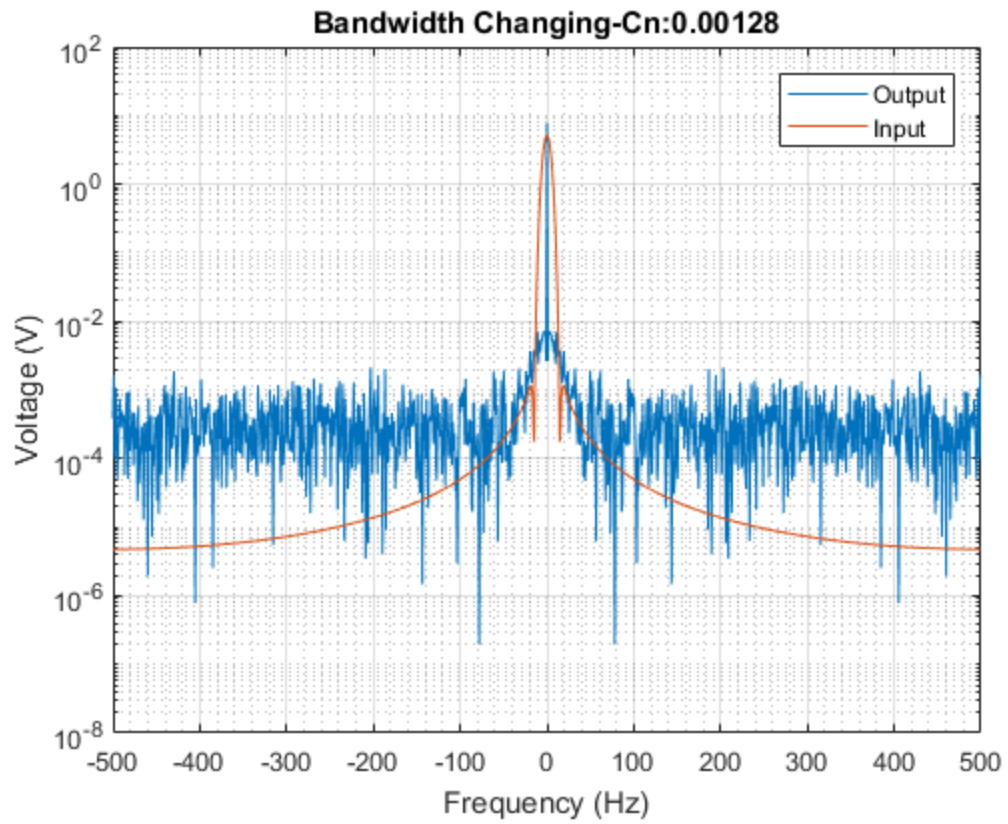

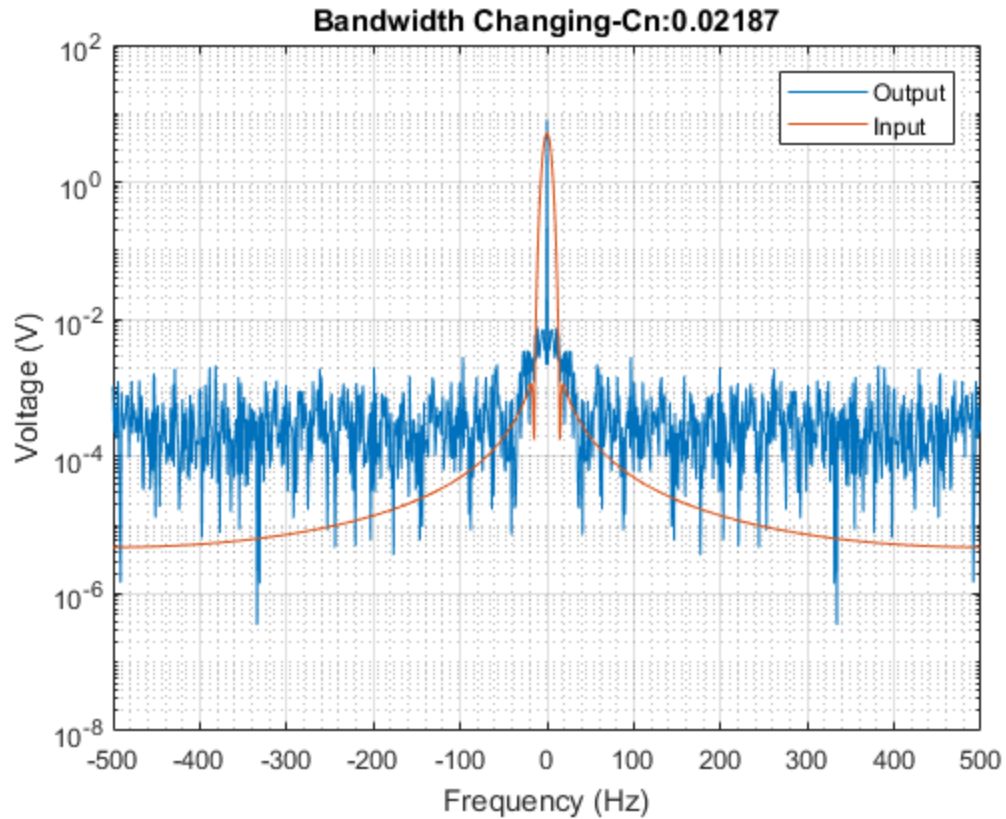

Part F) 2 Plots with different time steps

Can see that with larger time steps the accuracy of the plot suffers and less data points are taken not giving good insight into the true signal that is occurring

$C_n = 0.00001;$

```
C = [ 0 0 0 0 0 0 0 0 0;
      -Cx Cx 0 0 0 0 0 0;
      0 0 -L 0 0 0 0 0;
      0 0 0 0 0 0 0 0;
      0 0 0 0 0 0 0 0;
      0 0 0 0 0 0 0 0;
      0 0 0 -Cn 0 0 0 0;
      0 0 0 0 0 0 0 0];

G = [ 1 0 0 0 0 0 0 0;
      -G2 G1+G2 -1 0 0 0 0 0;
      0 1 0 -1 0 0 0 0;
      0 0 -1 G3 0 0 0 0;
      0 0 0 0 -Alpha 1 0 0;
      0 0 0 G3 -1 0 0 1;
      0 0 0 0 0 -G4 G4+G0 0;
      0 0 0 0 0 0 0 1];
```

```
for zz = 1:2


    deltaT = 0.001*zz^5;
    A = (C/deltaT + G);
    F = [0; 0; 0; 0; 0; 0; 0; 0; 0];
    Vold = [1; 0; 0; 0; 0; 0; 0; 0; 0];
    counter = 1;
    for i = 0.001:deltaT:L*0.001
        F(1) = normpdf(i,0.06,0.03)/13.2981;
        F(8) = normrnd(0.001, 0.0002);
        vNew = inv(A)*(C*Vold./deltaT + F);
        Vold = vNew;
        out(counter , 1) = i;
        out(counter , 2) = vNew(7);
        out(counter , 3) = vNew(1);
        counter = counter + 1;
    end
    figure;
    hold on;
    grid on;
    grid minor;
    title(strcat('Delta Time:', num2str(deltaT)));
    xlabel('Time (s)');
    ylabel('Voltage (V)');
    plot(out(:,1), out(:,2));
    plot(out(:,1), out(:,3));
    legend('Output', 'Input');
    hold off;



    figure;


    Fs = 1000;

    n = 2^nextpow2(L);
    Y = fft(out(:,2),n);
    Y = fftshift(Y);
    fshift = (-n/2:n/2-1)*(Fs/n);
    powershift = abs(Y).^2/n;
    f = Fs*(0:(n/2))/n;
    P = abs(Y/n);
    semilogy(fshift, powershift) ;
    hold on;
    grid on;
    grid minor;
    title(strcat('Delta Time:', num2str(deltaT)));
    xlabel('Frequency (Hz)');
    ylabel('Voltage (V)');
    Y = fft(out(:,3),n);
```

```
Y = fftshift(Y);  
fshift = (-n/2:n/2-1)*(Fs/n);  
powershift = abs(Y).^2/n;  
f = Fs*(0:(n/2))/n;  
P = abs(Y/n);  
semilogy(fshift, powershift) ;  
legend('Output', 'Input');  
hold off;  
end
```

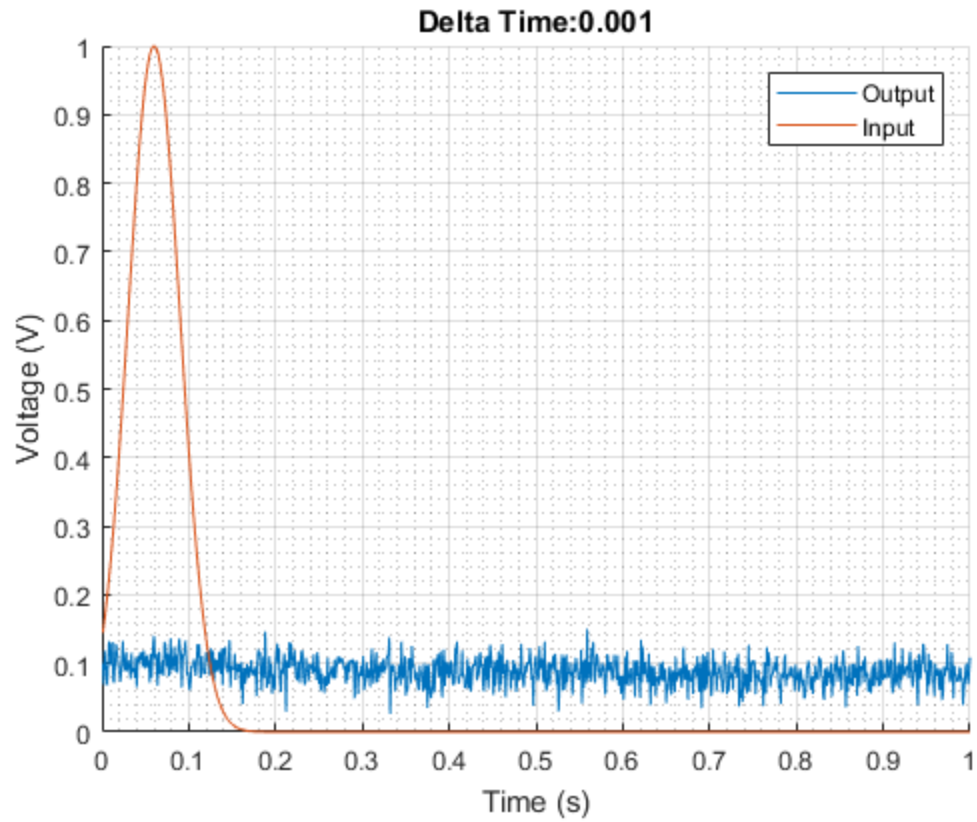

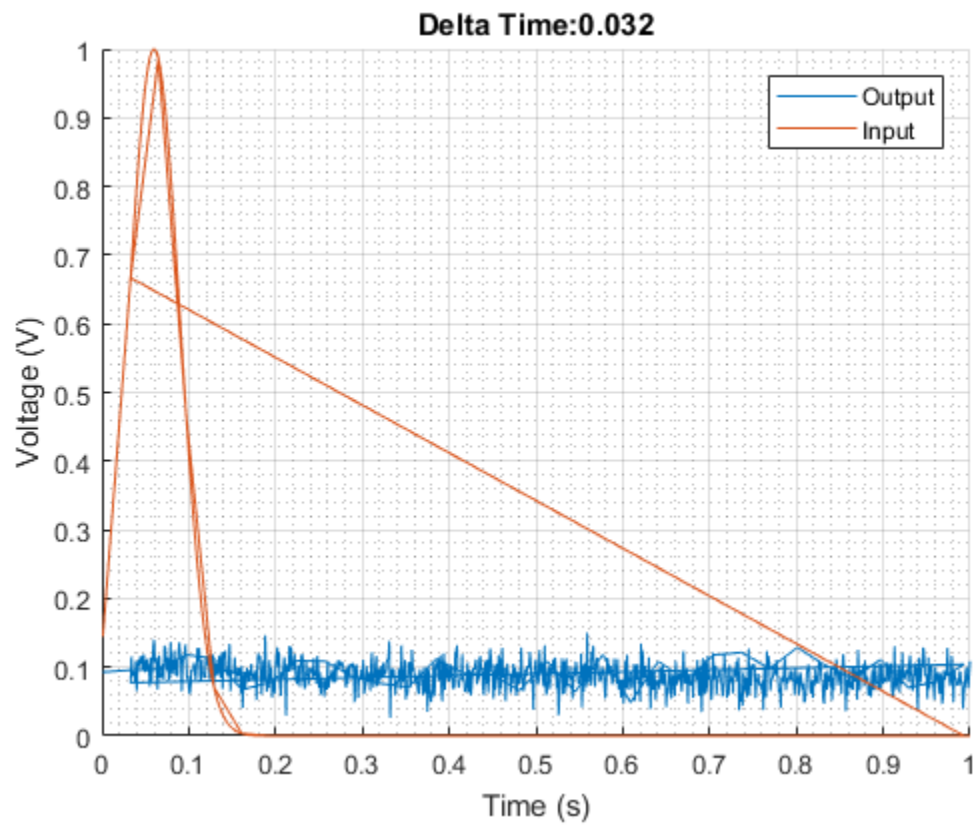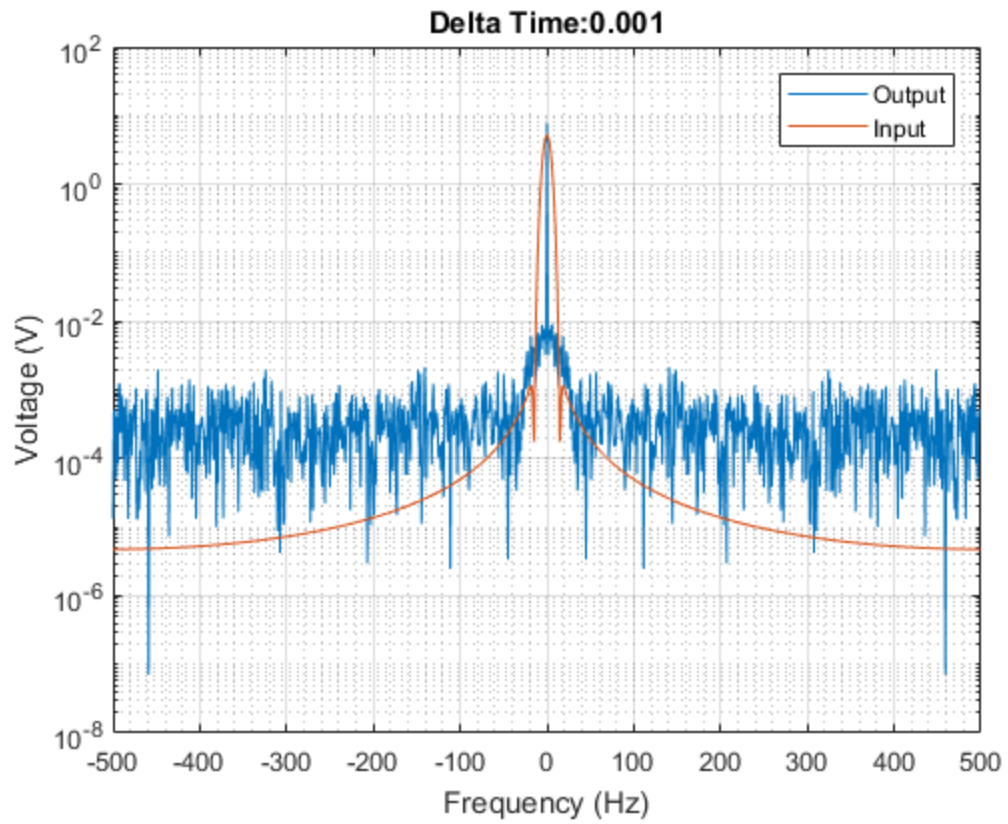

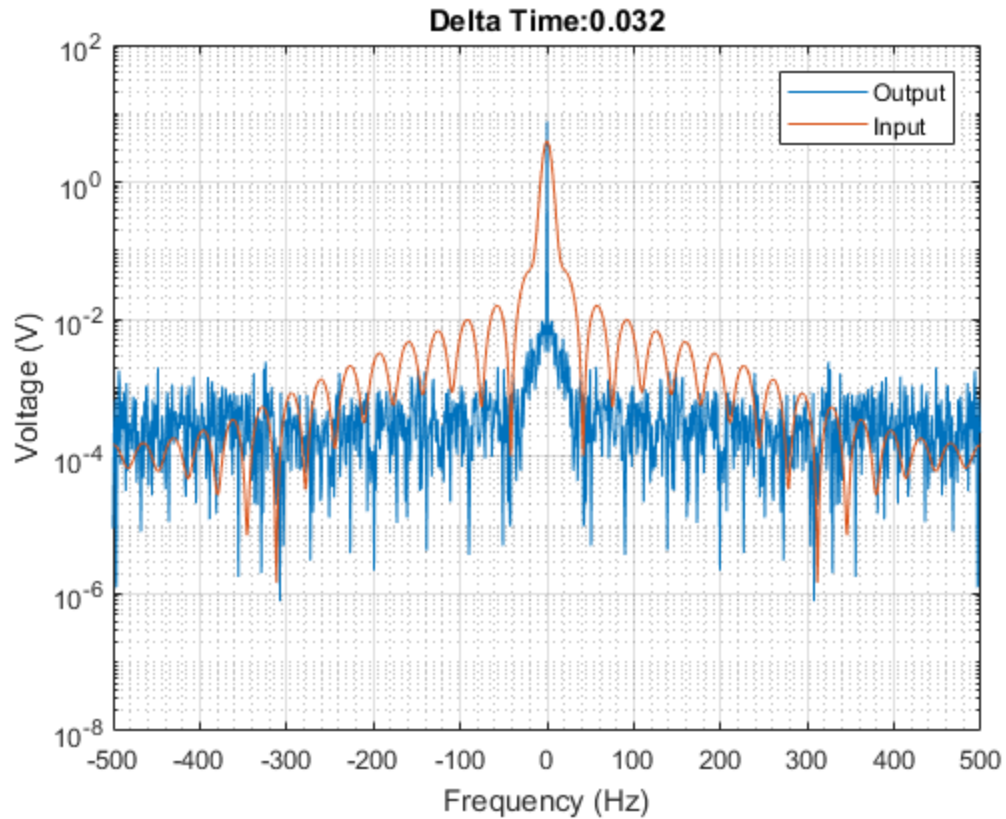

Question 4

Part A) Change to Simulator

In order to account for nonlinear terms one would need to incorporate an additional matrix. In the notes this matrix is defined as the B matrix and is represented by the following equation.

$$V^{\{j\}} = A^{-1} \left[C \frac{V^{\{j-1\}}}{\Delta t} + F(t^{\{j\}}) - B(V^{\{j\}}) \right]$$

This could be implemented by changing the equation that relates to calculating the new V matrix when using the old V matrix. The B matrix would include the squared and cubed term by multiplying the V matrix into the B.

Published with MATLAB® R2017a